

Seven-Segment Display

高政 11912015


一、简述

a) 实验目的

通过本次实验了解七段数字显示器的工作原理，继续熟悉模块化设计的 VHDL 设计理念。

b) 七段显示码


本次实验使用的是共阳极的七段数字显示器，其电路结构如下

 

同一时刻拉高二极管阳极并将相应的阴极拉低即可显示数字，应用 4-8 解码器可实现对阴极型号的控制，解码格式如下


x	a	b	c	d	e	f	g	
0	0	0	0	0	0	0	1	
1	1	0	0	1	1	1	1	
2	0	0	1	0	0	1	0	
3	0	0	0	0	1	1	0	1 = off
4	1	0	0	1	1	0	0	0 = on
5	0	1	0	0	1	0	0	
6	0	1	0	0	0	0	0	
7	0	0	0	1	1	1	1	
8	0	0	0	0	0	0	0	
9	0	0	0	0	1	0	0	
A	0	0	0	1	0	0	0	
B	1	1	0	0	0	0	0	
C	0	1	1	0	0	0	1	
D	1	0	0	0	0	1	0	
E	0	1	1	0	0	0	0	
F	0	1	1	1	0	0	0	

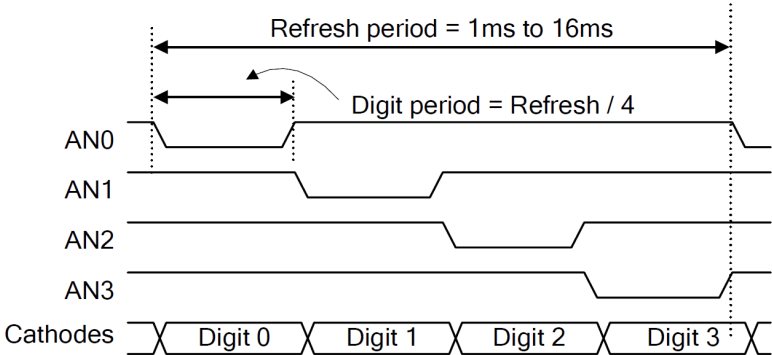为节省引脚数量，本实验板上的八个数字显示器共用一组阴极信号，为实现八个显示器显示不同的数字，采取同一时刻仅拉高一个显示器的阳极，利用人眼的视觉残留效应，以至少每秒 45Hz 的频率循环拉高各个显示器达到同时显示不同数字的效果，阳极信号循环示例如下



二、实验准备

计数器部分的 RTL 设计原理如下

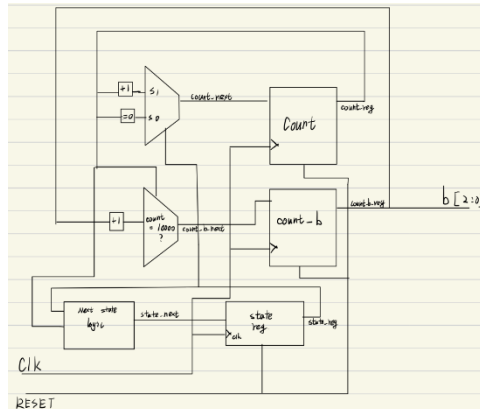

三、VHDL 代码与 testbench 代码

a) 计数器模块

VHDL 代码:

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use ieee.std_logic_arith.all;

use ieee.std_logic_unsigned.all;

entity counter is

Port (CLK : in STD_LOGIC;

RESET : in STD_LOGIC;

b : out STD_LOGIC_VECTOR (2 downto 0));

end counter;

architecture Behavioral of counter is

type state_type is(s0, s1);

signal state, state_next :state_type;

signal count, count_next : std_logic_vector(13 downto 0);

signal count_b, count_b_next: std_logic_vector(2 downto 0);

constant upcount :integer:=10000;

begin

clk_pro:process(CLK, RESET)is

begin

if RESET = '1' then

state <= s0;

count <= (others => '0');

count_b <= "000";

elsif(CLK'event and CLK = '1') then

state <= state_next;

count <= count_next;

count_b <= count_b_next;

end if;

end process;

```

process (state, state_next, count, count_next) is
begin
    state_next <= s0;
    count_next <= count;
    case state is
        when s0 =>
            count_next <= (others => '0');
            count_b_next <= count_b + 1;
            state_next <= s1;
        when s1 =>
            if count = upcount - 2 then
                count_next <= (others => '0');
                state_next <= s0;
            else
                count_next <= count + 1;
                state_next <= s1;
            end if;
        end case;
    end process;
    b <= count_b;
end Behavioral;

```

testbench 代码:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity tb_count is
end tb_count;

architecture Behavioral of tb_count is
    component counter
    port(
        CLK : in STD_LOGIC;
        RESET : in STD_LOGIC;
        b : out STD_LOGIC_VECTOR (2 downto 0)
    );
    end component;

    signal CLK : std_logic:='0';
    signal RESET : std_logic:='0';

    signal b : std_logic_vector(2 downto 0):="000";

    constant per : time:= 100 ns;

```

```

begin
uut:counter
port map(
    CLK => CLK,
    RESET => RESET,
    b => b
);

```

```

clk_pro:process
begin
    CLK <= '0';
    wait for per/2;
    CLK <= '1';
    wait for per/2;
end process;

```

```

reset_pro:process
begin
    RESET <= '1';
    for i in 1 to 2 loop
        wait until CLK = '1';
    end loop;
    RESET <= '0';
    wait;
end process;
end Behavioral;

```

b) 阳极信号产生模块

VHDL 代码:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity anode_driver is
    Port ( b : in std_logic_vector(2 downto 0);
          AN0 : out STD_LOGIC;
          AN1 : out STD_LOGIC;
          AN2 : out STD_LOGIC;
          AN3 : out STD_LOGIC;
          AN4 : out STD_LOGIC;
          AN5 : out STD_LOGIC;
          AN6 : out STD_LOGIC;
          AN7 : out STD_LOGIC);
end anode_driver;

```

architecture Behavioral of anode_driver is

```

begin
process(b) is
begin
    AN0 <= '1';
    AN1 <= '1';
    AN2 <= '1';
    AN3 <= '1';
    AN4 <= '1';
    AN5 <= '1';
    AN6 <= '1';
    AN7 <= '1';
    case b is
    when "000" =>
        AN0 <= '0';
    when "001" =>
        AN1 <= '0';
    when "010" =>
        AN2 <= '0';
    when "011" =>
        AN3 <= '0';
    when "100" =>
        AN4 <= '0';
    when "101" =>
        AN5 <= '0';
    when "110" =>
        AN6 <= '0';
    when "111" =>
        AN7 <= '0';
    when others =>
    end case;
end process;
end Behavioral;

```

testbench 代码:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.std_logic_signed.all;
use IEEE.std_logic_unsigned.all;

entity tb_anode_driver is
end tb_anode_driver;

architecture Behavioral of tb_anode_driver is
    component anode_driver is

```

```

Port ( b : in std_logic_vector(2 downto 0);
      AN0 : out STD_LOGIC;
      AN1 : out STD_LOGIC;
      AN2 : out STD_LOGIC;
      AN3 : out STD_LOGIC;
      AN4 : out STD_LOGIC;
      AN5 : out STD_LOGIC;
      AN6 : out STD_LOGIC;
      AN7 : out STD_LOGIC);
end component;

signal b : std_logic_vector(2 downto 0):="000";

signal AN0, AN1, AN2, AN3, AN4, AN5, AN6, AN7: std_logic:='1';

constant per : time:= 100 ns;

begin
 uut: anode_driver
port map(
  b => b,
  AN0 => AN0,
  AN1 => AN1,
  AN2 => AN2,
  AN3 => AN3,
  AN4 => AN4,
  AN5 => AN5,
  AN6 => AN6,
  AN7 => AN7
);

b_pro : process
begin
  b <= b + 1;
  wait for per;
end process;
end Behavioral;

```

c) 输入选择模块

VHDL 代码:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.std_logic_signed.all;

```

entity mux is

```

Port ( char1 : in STD_LOGIC_VECTOR (3 downto 0);
      char2 : in STD_LOGIC_VECTOR (3 downto 0);
      char3 : in STD_LOGIC_VECTOR (3 downto 0);
      char4 : in STD_LOGIC_VECTOR (3 downto 0);
      b : in STD_LOGIC_VECTOR (2 downto 0);
      x : out STD_LOGIC_VECTOR (3 downto 0));
end mux;

```

architecture Behavioral of mux is

begin

mux_pro:process(char1, char2, char3, char4, b)is

begin

```

x <= "0000";
case b is
when "000" =>
    x <= char1;
when "001" =>
    x <= char2;
when "010" =>
    x <= char3;
when "011" =>
    x <= char4;
when "100" =>
    x <= char1 + char2;
when "101" =>
    x <= char1 - char2;
when "110" =>
    x <= char3 + char4;
when "111" =>
    x <= char3 - char4;
when others =>
end case;

```

end process;

end Behavioral;

testbench 代码:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.std_logic_signed.all;
use IEEE.std_logic_unsigned.all;

```

entity tb_mux is

end tb_mux;

architecture Behavioral of tb_mux is

component mux is

```
Port (  
    char1 : in STD_LOGIC_VECTOR (3 downto 0);  
    char2 : in STD_LOGIC_VECTOR (3 downto 0);  
    char3 : in STD_LOGIC_VECTOR (3 downto 0);  
    char4 : in STD_LOGIC_VECTOR (3 downto 0);  
    b : in STD_LOGIC_VECTOR (2 downto 0);  
    x : out STD_LOGIC_VECTOR (3 downto 0)  
);  
end component;
```

```
signal char1: std_logic_vector(3 downto 0):="0001";  
signal char2: std_logic_vector(3 downto 0):="0010";  
signal char3: std_logic_vector(3 downto 0):="0011";  
signal char4: std_logic_vector(3 downto 0):="0100";  
signal b: std_logic_vector(2 downto 0):="000";
```

```
signal x: std_logic_vector(3 downto 0):="0000";
```

```
constant per : time:= 100 ns;
```

```
begin  
    uut:mux  
    port map(  
        char1 => char1,  
        char2 => char2,  
        char3 => char3,  
        char4 => char4,  
        b => b,  
        x => x  
    );
```

```
b_pro : process  
begin  
    b <= b + 1;  
    wait for per;  
end process;
```

```
end Behavioral;
```

d) 阴极信号产生模块

VHDL 代码:

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.std_logic_signed.all;
```



```
use IEEE.std_logic_unsigned.all;
```

```
entity hex7seg is
```

```
    Port ( x : in STD_LOGIC_VECTOR (3 downto 0);
```

```
          LED : out STD_LOGIC_VECTOR (7 downto 0));
```

```
end hex7seg;
```

```
architecture Behavioral of hex7seg is
```

```
begin
```

```
process(x) is
```

```
begin
```

```
    LED <= "00000000";
```

```
    case x is
```

```
        when "0000" =>
```

```
            LED <= "00000011";
```

```
        when "0001" =>
```

```
            LED <= "10011111";
```

```
        when "0010" =>
```

```
            LED <= "00100101";
```

```
        when "0011" =>
```

```
            LED <= "00001101";
```

```
        when "0100" =>
```

```
            LED <= "10011001";
```

```
        when "0101" =>
```

```
            LED <= "01001001";
```

```
        when "0110" =>
```

```
            LED <= "01000001";
```

```
        when "0111" =>
```

```
            LED <= "00011111";
```

```
        when "1000" =>
```

```
            LED <= "00000001";
```

```
        when "1001" =>
```

```
            LED <= "00001001";
```

```
        when "1010" =>
```

```
            LED <= "00010001";
```

```
        when "1011" =>
```

```
            LED <= "11000001";
```

```
        when "1100" =>
```

```
            LED <= "01100011";
```

```
        when "1101" =>
```

```
            LED <= "10000101";
```

```
        when "1110" =>
```

```
            LED <= "01100001";
```

```
        when "1111" =>
```

```

        LED <= "01110001";
    when others =>
        end case;
end process;
end Behavioral;

```

testbench 代码:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.std_logic_signed.all;
use IEEE.std_logic_unsigned.all;

```

```

entity tb_hex7seg is
end tb_hex7seg;

```

architecture Behavioral of tb_hex7seg is

```

    component hex7seg
    port(
        x : in std_logic_vector (3 downto 0);
        LED : out std_logic_vector (7 downto 0)
    );
end component;

```

```

    signal x : std_logic_vector(3 downto 0):="0000";

```

```

    signal LED : std_logic_vector(7 downto 0):="00000000";

```

```

    constant per : time:= 100 ns;

```

```

begin
    uut: hex7seg
    port map(
        x => x,
        LED => LED
    );

```

```

x_pro:process
begin
    x <= x + 1;
    wait for per;
end process;
end Behavioral;

```

e) 顶层设计

VHDL 代码:

```

library IEEE;

```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity seven_segment_display is
```

```
    Port ( CLK : in STD_LOGIC;  
           RESET : in STD_LOGIC;  
           char1 ,char2 ,char3 ,char4 : in STD_LOGIC_VECTOR (3 downto 0);  
           LED : out STD_LOGIC_VECTOR (7 downto 0);  
           AN0 ,AN1 ,AN2 ,AN3 ,AN4 ,AN5 ,AN6 ,AN7 : out STD_LOGIC);
```

```
end seven_segment_display;
```

```
architecture Behavioral of seven_segment_display is
```

```
    component mux is
```

```
        Port (  
            char1 ,char2 ,char3 ,char4 : in STD_LOGIC_VECTOR (3 downto 0);  
            b : in STD_LOGIC_VECTOR (2 downto 0);  
            x : out STD_LOGIC_VECTOR (3 downto 0)
```

```
        );
```

```
    end component;
```

```
    component hex7seg
```

```
    port(  
        x : in STD_LOGIC_VECTOR (3 downto 0);  
        LED : out STD_LOGIC_VECTOR (7 downto 0)
```

```
    );
```

```
    end component;
```

```
    component counter is
```

```
        Port (  
            CLK : in STD_LOGIC;  
            RESET : in STD_LOGIC;  
            b : out STD_LOGIC_VECTOR (2 downto 0)
```

```
        );
```

```
    end component;
```

```
    component anode_driver is
```

```
        Port (  
            b : in std_logic_vector(2 downto 0);  
            AN0 ,AN1 ,AN2 ,AN3 ,AN4 ,AN5 ,AN6 ,AN7 : out STD_LOGIC
```

```
        );
```

```
    end component;
```

```
    signal b:std_logic_vector(2 downto 0);
```

```
    signal x:std_logic_vector(3 downto 0);
```

```

begin
mux_pro:mux
port map(
    char1 => char1,
    char2 => char2,
    char3 => char3,
    char4 => char4,
    b => b,
    x => x
);

hex7seg_pro:hex7seg
port map(
    x => x,
    LED => LED
);

counter_pro: counter
port map(
    CLK => CLK,
    RESET => RESET,
    b => b
);

anode_driver_pro: anode_driver
port map(
    b => b,
    AN0 => AN0,
    AN1 => AN1,
    AN2 => AN2,
    AN3 => AN3,
    AN4 => AN4,
    AN5 => AN5,
    AN6 => AN6,
    AN7 => AN7
);
end Behavioral;

```

testbench 代码:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.std_logic_signed.all;
use IEEE.std_logic_unsigned.all;

```

entity tb_seven_segment_display is

```
end tb_seven_segment_display;
```

```
architecture Behavioral of tb_seven_segment_display is
```

```
    component seven_segment_display is
```

```
    Port (
```

```
        CLK : in STD_LOGIC;
```

```
        RESET : in STD_LOGIC;
```

```
        char1 ,char2 ,char3 ,char4 : in STD_LOGIC_VECTOR (3 downto 0);
```

```
        LED : out STD_LOGIC_VECTOR (7 downto 0);
```

```
        AN0 ,AN1 ,AN2 ,AN3 ,AN4 ,AN5 ,AN6 ,AN7 : out STD_LOGIC
```

```
    );
```

```
end component;
```

```
    signal CLK, RESET: std_logic:= '0';
```

```
    signal char1: std_logic_vector(3 downto 0):= "0001";
```

```
    signal char2: std_logic_vector(3 downto 0):= "0010";
```

```
    signal char3: std_logic_vector(3 downto 0):= "0011";
```

```
    signal char4: std_logic_vector(3 downto 0):= "0100";
```

```
    signal LED: std_logic_vector(7 downto 0):= "00000000";
```

```
    signal AN0, AN1, AN2, AN3, AN4, AN5, AN6, AN7: std_logic:= '1';
```

```
    constant per : time:= 100 ns;
```

```
begin
```

```
    uut: seven_segment_display
```

```
    port map(
```

```
        CLK => CLK,
```

```
        RESET => RESET,
```

```
        char1 => char1,
```

```
        char2 => char2,
```

```
        char3 => char3,
```

```
        char4 => char4,
```

```
        LED => LED,
```

```
        AN0 => AN0,
```

```
        AN1 => AN1,
```

```
        AN2 => AN2,
```

```
        AN3 => AN3,
```

```
        AN4 => AN4,
```

```
        AN5 => AN5,
```

```
        AN6 => AN6,
```

```
        AN7 => AN7
```

```
    );
```

```


clk_pro:process
begin
    CLK <= '0';
    wait for per/2;
    CLK <= '1';
    wait for per/2;
end process;

reset_pro:process
begin
    RESET <= '1';
    for i in 1 to 2 loop
        wait until CLK = '1';
    end loop;
    RESET <= '0';
    wait;
end process;
end Behavioral;

```


四、实验结果与分析

a) 行为仿真

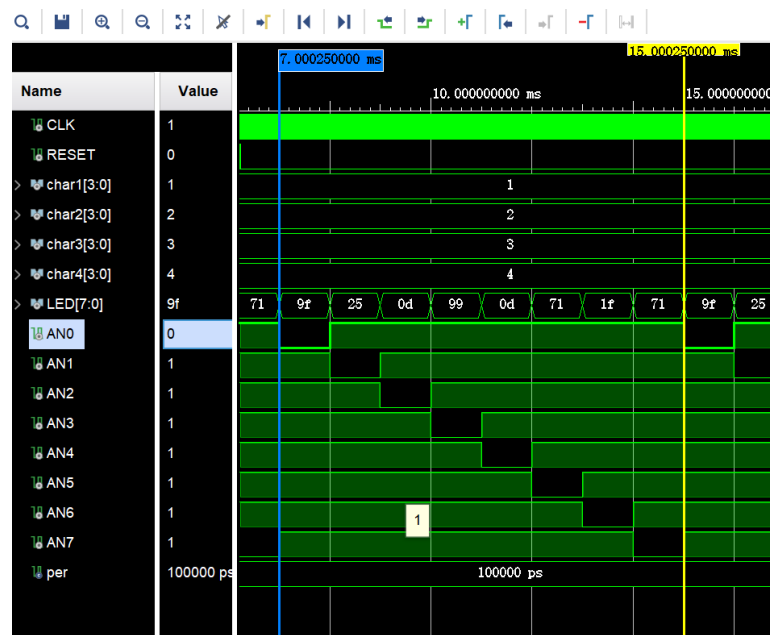


由图可知，程序功能正常。


b) 综合后功能仿真

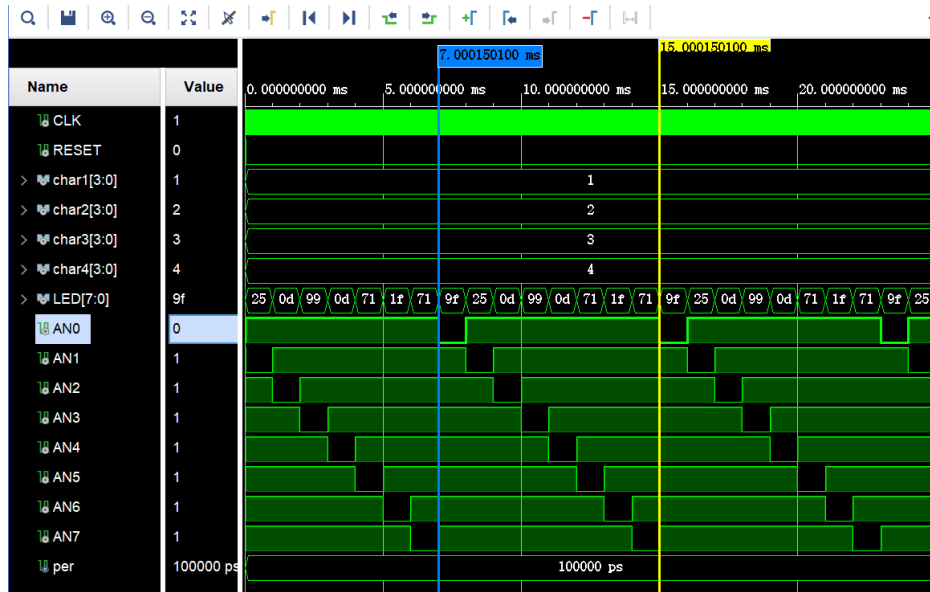


c) 综合后时序仿真

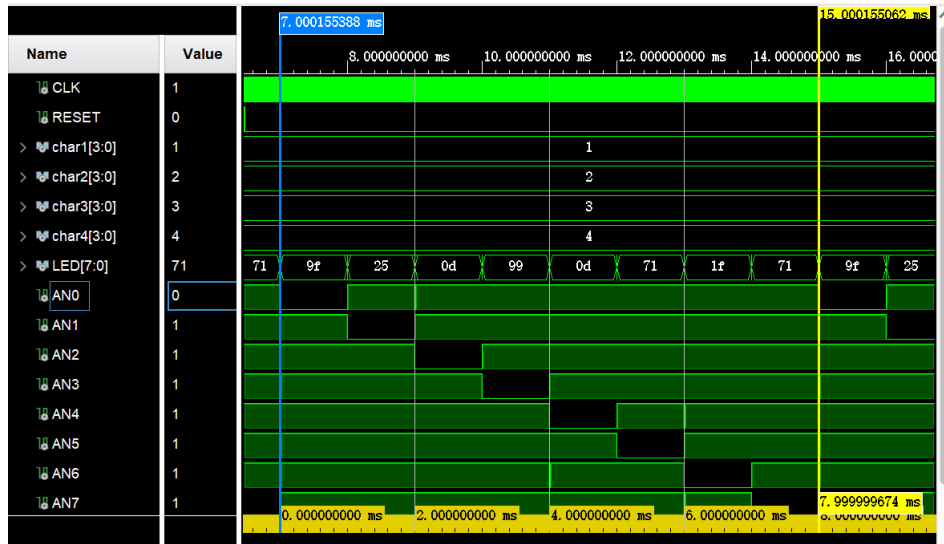


d) 布线后功能仿真

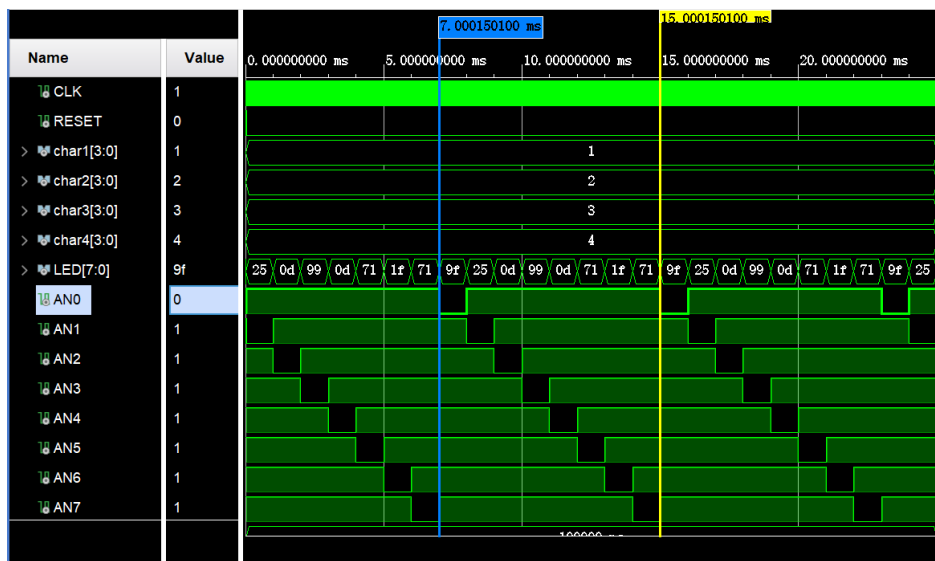


e) 布线后时序仿真

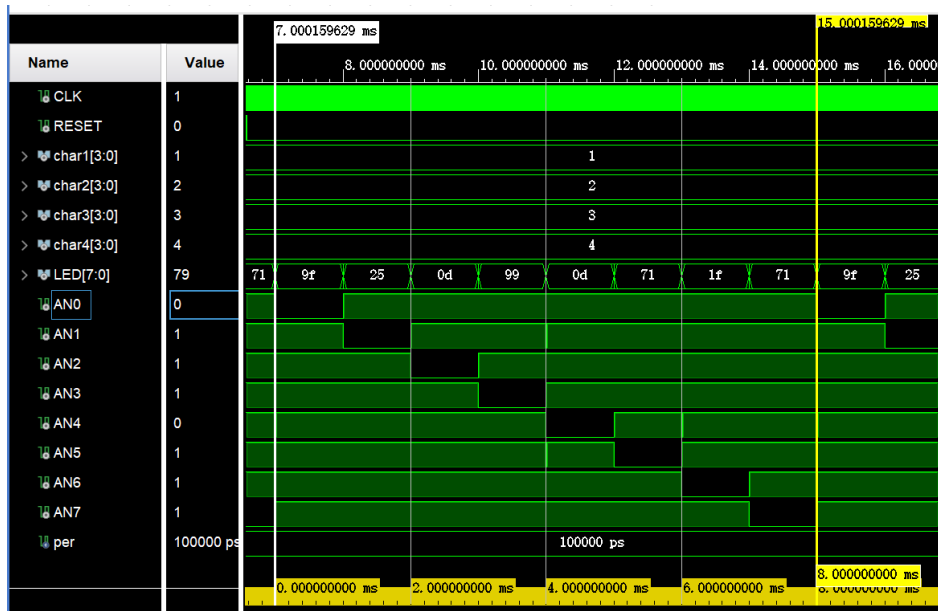

f) RTL 原理图

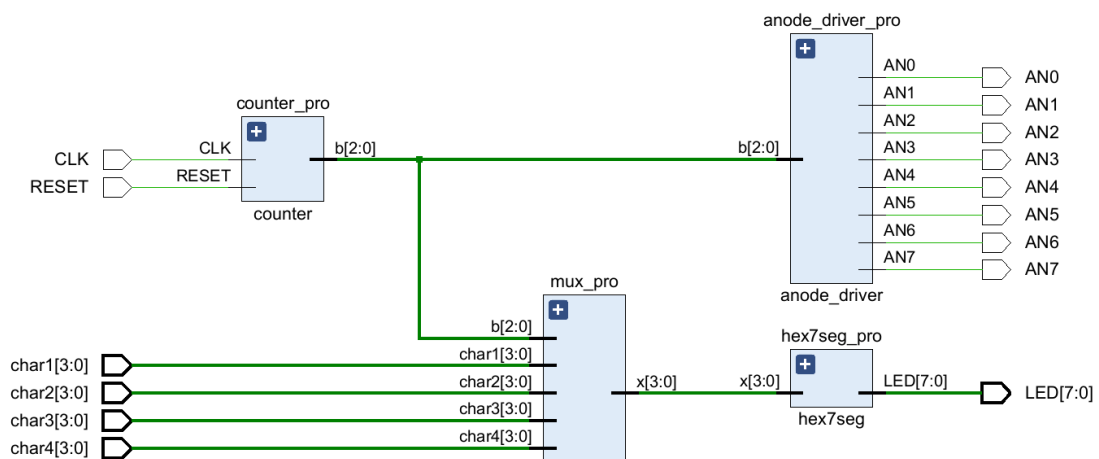

g) 上板实验结果

 

实验板实际效果如上，从左至右八个显示器分别显示：a, b, c, d, a + b, a - b, c + d, c - d。下方 16 个开关依次对应 a, b, c, d。

五、实验结论

实验结果符合预期，通过本次实验我站我了七段数字显示器的使用方式，对时序电路的设计更为熟练，对模块化设计的理念也有了更为深入的理解。